

Q1)

BCD stands for Binary Coded Decimal. In the BCD numbering system a decimal number is separated into four bits for each decimal digit within the number. Each decimal digit is represented by its weighted binary value performing a direct translation of the number. So a 4-bit group represents each displayed decimal digits from 0000 for a zero to 1001 for a nine. The inputs I_0 to I_9 represents decimal digits 0-9 respectively and the BCD corresponding to decimal digits are represented by bits $Out[3], Out[2], Out[1], Out[0]$.

Truth table :-

I_9	I_8	I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	$Out[3]$	$Out[2]$	$Out[1]$	$Out[0]$
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

The following boolean expressions are obtained from the above truth table :-

$$\text{Out}[0] = I_1 + I_3 + I_5 + I_7 + I_9$$

$$\text{Out}[1] = I_2 + I_3 + I_6 + I_7$$


$$\text{Out}[2] = I_4 + I_5 + I_6 + I_7$$


$$\text{Out}[3] = I_8 + I_9$$

the term $I_6 + I_7$ is common in $\text{Out}[1]$, $\text{Out}[2]$ so it is shared between $\text{Out}[1]$ and $\text{Out}[2]$


Now, we will implement the function using AND and OR gates. Later we will convert it into implementation using NAND, NOR, NOT gates.

Circuit Diagram:-

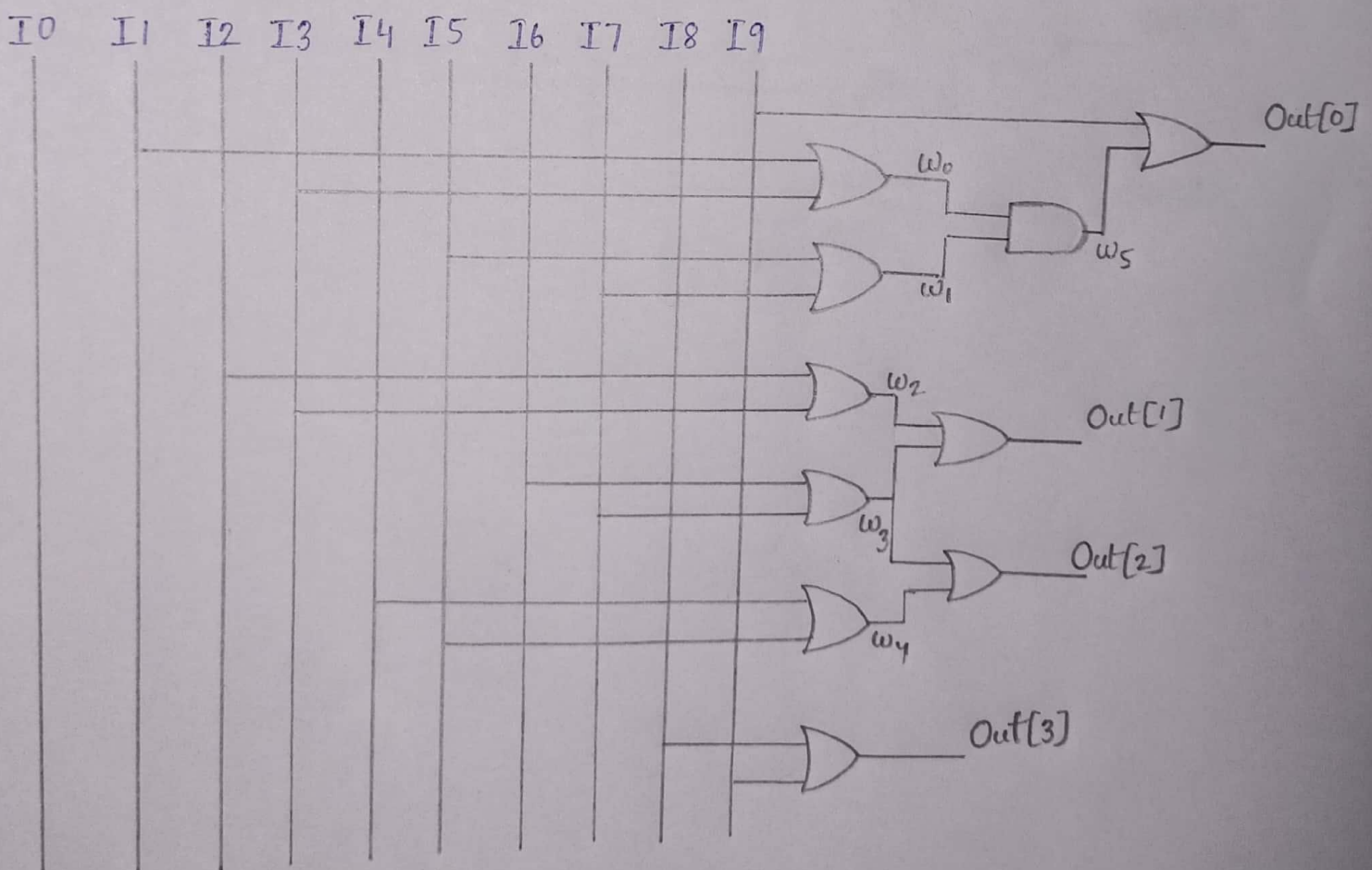

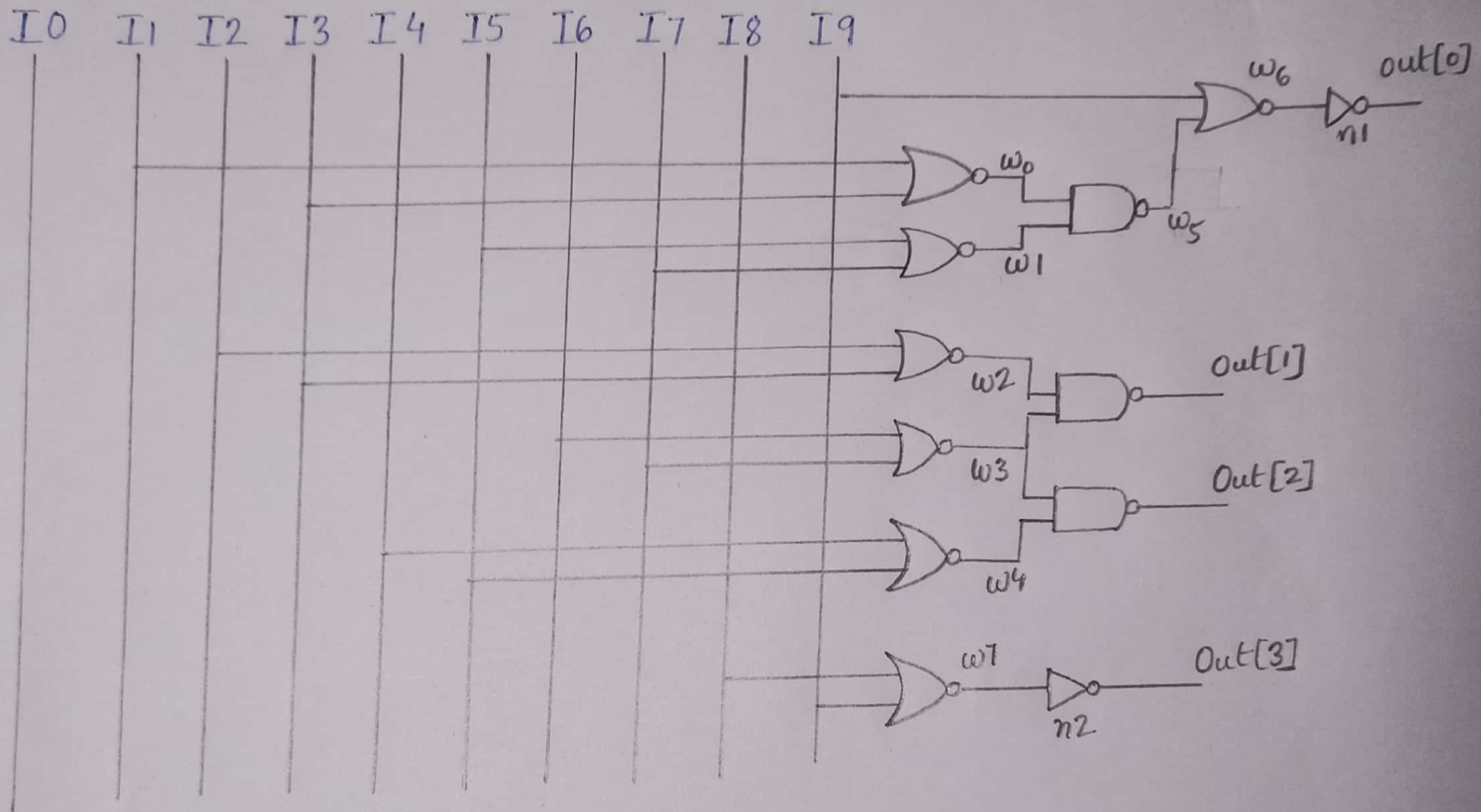

Q2)

 

The above figure shows the seven-segment display. If input to any segment is 1 then the segment glows. If input is 0 then the segment doesn't glow.

Truth Table :-

A3	A2	A1	A0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

Now we will use four variable K-map to minimize the seven outputs separately with respect to four inputs.

K-Map Minimization:-

a:-

A_3A_2	A_1A_0	\bar{A}_1A_0	A_1A_0	$\bar{A}_1\bar{A}_0$
$\bar{A}_3\bar{A}_2$	1		1	1
\bar{A}_3A_2		1	1	1
$A_3\bar{A}_2$	x	x	x	x
A_3A_2	1	1	x	x

$$a = \bar{A}_2\bar{A}_0 + A_3 + A_1 + A_2A_0$$

b:-

A_3A_2	A_1A_0	\bar{A}_1A_0	A_1A_0	$\bar{A}_1\bar{A}_0$
$\bar{A}_3\bar{A}_2$	1	1	1	1
\bar{A}_3A_2	1		1	
$A_3\bar{A}_2$	x	x	x	x
A_3A_2	1	1	x	x

$$b = \bar{A}_2 + \bar{A}_1\bar{A}_0 + A_1A_0$$

c:-

A_3A_2	A_1A_0	\bar{A}_1A_0	A_1A_0	$\bar{A}_1\bar{A}_0$
$\bar{A}_3\bar{A}_2$	1	1	1	
\bar{A}_3A_2	1	1	1	1
$A_3\bar{A}_2$	x	x	x	x
A_3A_2	1	1	x	x

$$c = \bar{A}_1 + A_0 + A_2$$

d:-

A_3A_2	A_1A_0	\bar{A}_1A_0	A_1A_0	$\bar{A}_1\bar{A}_0$
$\bar{A}_3\bar{A}_2$	1		1	1
\bar{A}_3A_2		1		1
$A_3\bar{A}_2$	x	x	x	x
A_3A_2	1	1	x	x

$$d = \bar{A}_2\bar{A}_0 + A_3 + A_1\bar{A}_0 + A_1\bar{A}_2 + A_2\bar{A}_1$$

e:-

A_3A_2	A_1A_0	\bar{A}_1A_0	A_1A_0	$\bar{A}_1\bar{A}_0$
$\bar{A}_3\bar{A}_2$	1			1
\bar{A}_3A_2				1
$A_3\bar{A}_2$	x	x	x	x
A_3A_2	1		x	x

$$e = \bar{A}_2\bar{A}_0 + A_1\bar{A}_0$$

f:-

A_3A_2	A_1A_0	\bar{A}_1A_0	A_1A_0	$\bar{A}_1\bar{A}_0$
$\bar{A}_3\bar{A}_2$	1			
\bar{A}_3A_2	1	1		1
$A_3\bar{A}_2$	x	x	x	x
A_3A_2	1	1	x	x

$$f = \bar{A}_1\bar{A}_0 + A_3 + A_2A_0 + A_2\bar{A}_1$$


g:-

A_3A_2	A_1A_0	\bar{A}_1A_0	A_1A_0	$\bar{A}_1\bar{A}_0$
$\bar{A}_3\bar{A}_2$			1	1
\bar{A}_3A_2	1	1		1
$A_3\bar{A}_2$	x	x	x	x
A_3A_2	1	1	x	x


$$g = A_3 + A_1\bar{A}_2 + A_2\bar{A}_0 + A_2\bar{A}_1$$

Now we will implement using AND, OR gates. Later we will implement using gates (NAND, NOR, NOT, XOR, XNOR)

Circuit Diagram:-

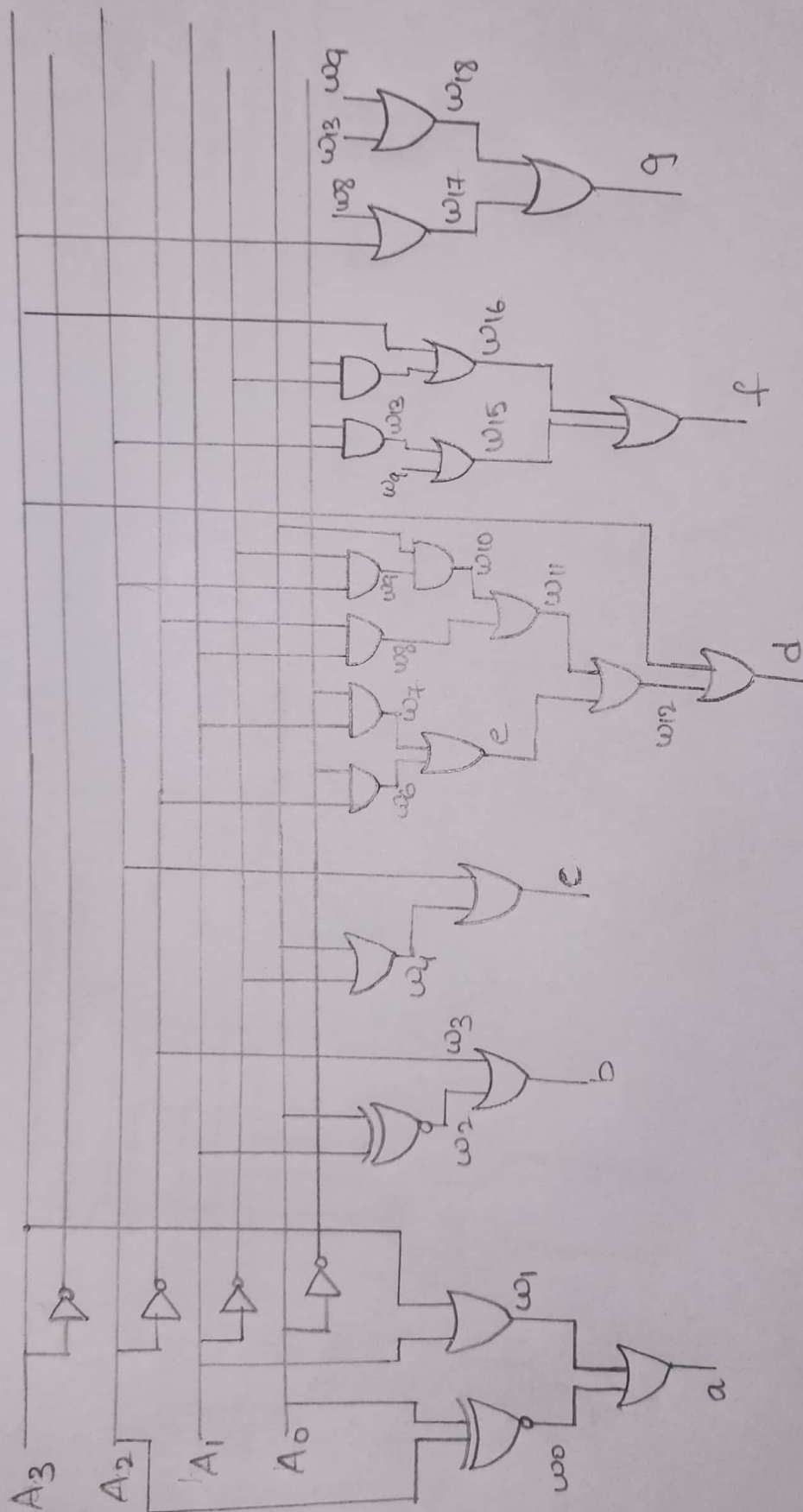

Structural:-

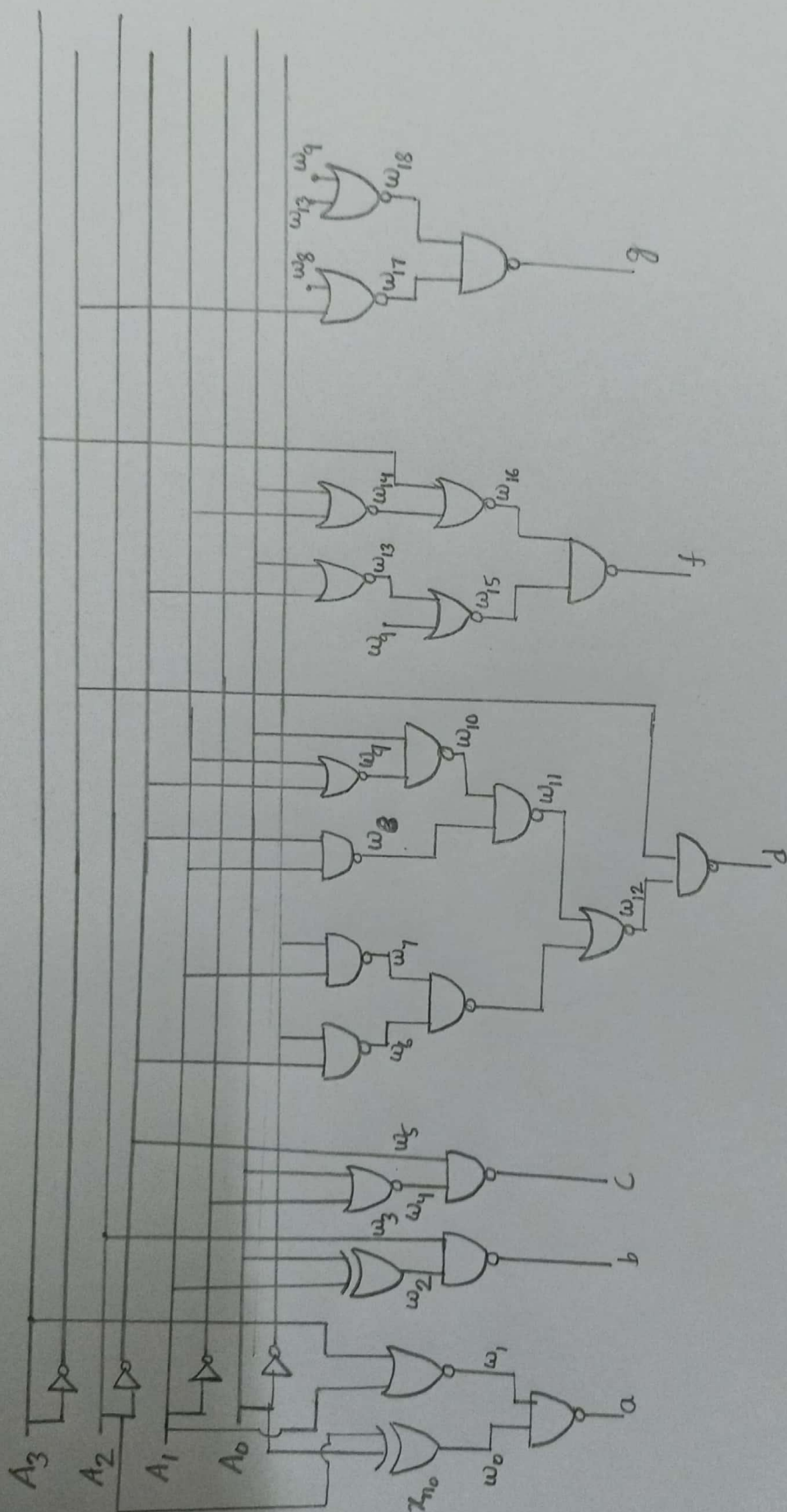

3) Let the BCD representation of x and y be.

$$x = x_3 x_2 x_1 x_0$$

$$y = y_3 y_2 y_1 y_0$$

case (i) $x = y$.

let f_0 be the function that represent $x = y$.

This case is possible when all bits in BCD representation of x and y are same, i.e.,

$$x_3 = y_3 \text{ and } x_2 = y_2 \text{ and } x_1 = y_1 \text{ and } x_0 = y_0$$

This can be written as.

$$\begin{aligned} f_0 &= (x_3 \odot y_3)(x_2 \odot y_2)(x_1 \odot y_1)(x_0 \odot y_0) \\ &= \overline{(x_3 \odot y_3)(x_2 \odot y_2) + (x_1 \odot y_1)(x_0 \odot y_0)} \end{aligned}$$

case (ii) $x < y$.

let f_2 be function that represent $x < y$.

This is possible when.

$x_3 < y_3$ (i), $(x_3 = y_3)$ and $x_2 < y_2$ (ii) $x_3 = y_3$ and $x_2 = y_2$ and $x_1 < y_1$ (iii) $x_3 = y_3$ and $x_2 = y_2$ and $x_1 = y_1$ and $x_0 < y_0$

$$\begin{aligned} f_2 &= \bar{x}_3 y_3 + (x_3 \odot y_3) \bar{x}_2 y_2 + (x_3 \odot y_3)(x_2 \odot y_2) \bar{x}_1 y_1 \\ &\quad + (x_3 \odot y_3)(x_2 \odot y_2)(x_1 \odot y_1) \bar{x}_0 y_0 \end{aligned}$$


case (iii) $x > y$.

let f_1 be function that represent $x > y$.


$$\begin{aligned} f_1 &= x_3 \bar{y}_3 + (x_3 \odot y_3) x_2 \bar{y}_2 + (x_3 \odot y_3)(x_2 \odot y_2) x_1 \bar{y}_1 \\ &\quad + (x_3 \odot y_3)(x_2 \odot y_2)(x_1 \odot y_1) x_0 \bar{y}_0 \end{aligned}$$

Circuit Diagram.


f_0

 

 
converting to the required gates, we get.




f_1

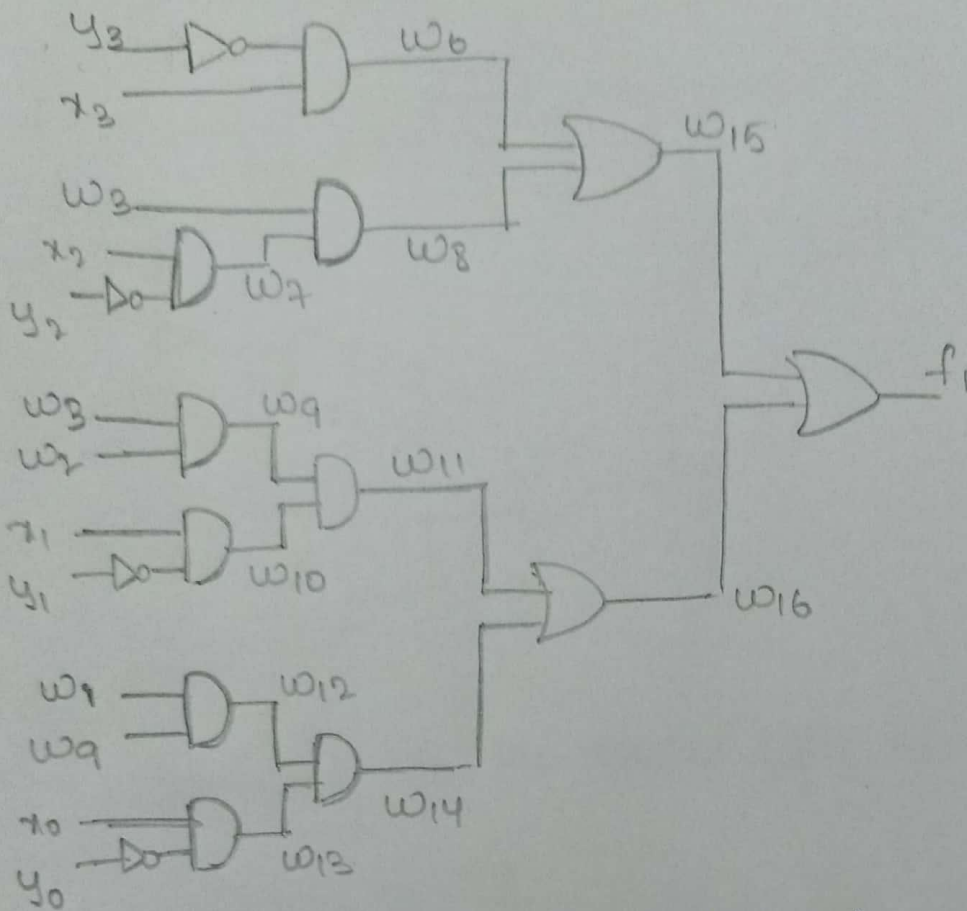

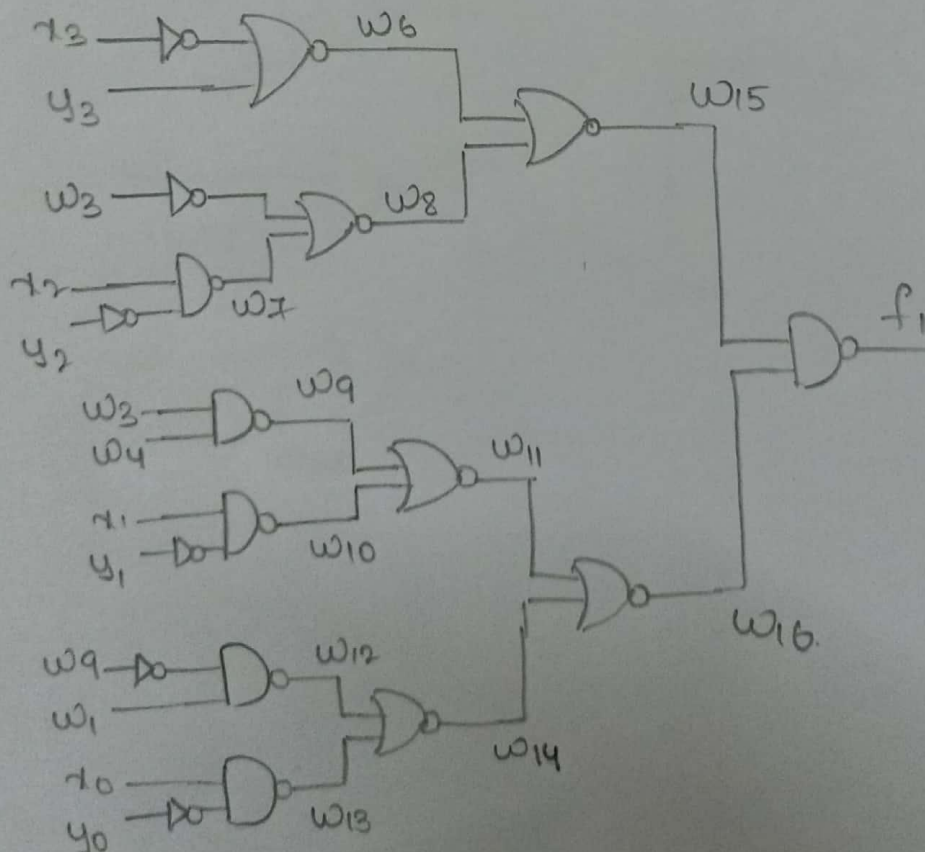
converting to the required gates, we get.




f_2

 


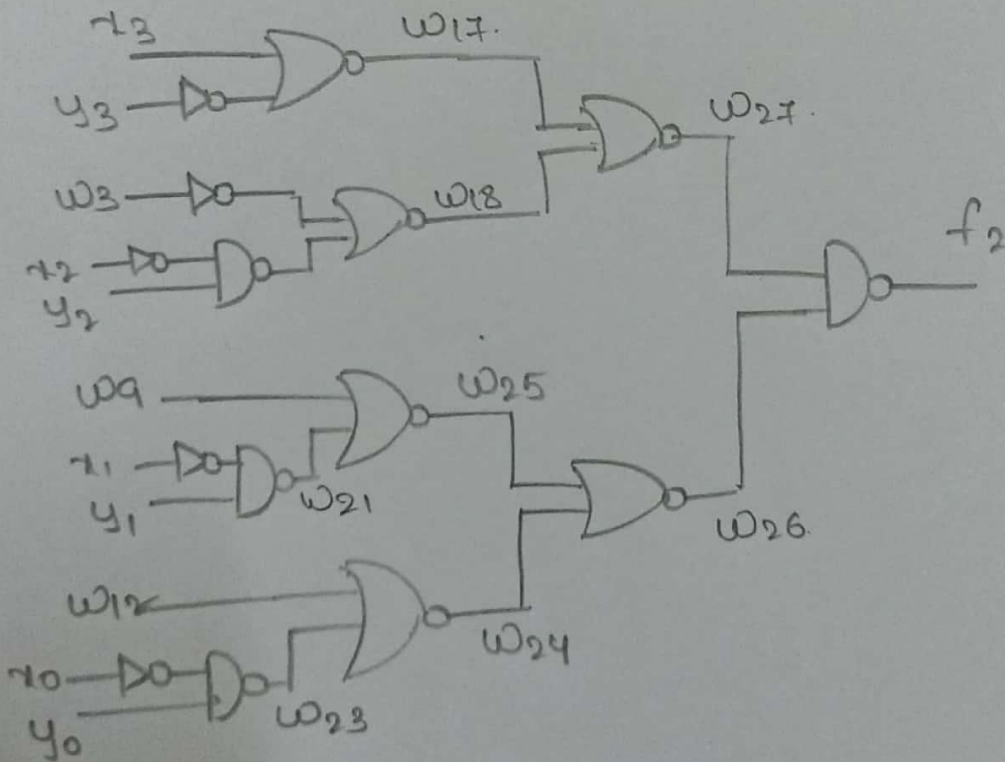converting to the required gates, we get.



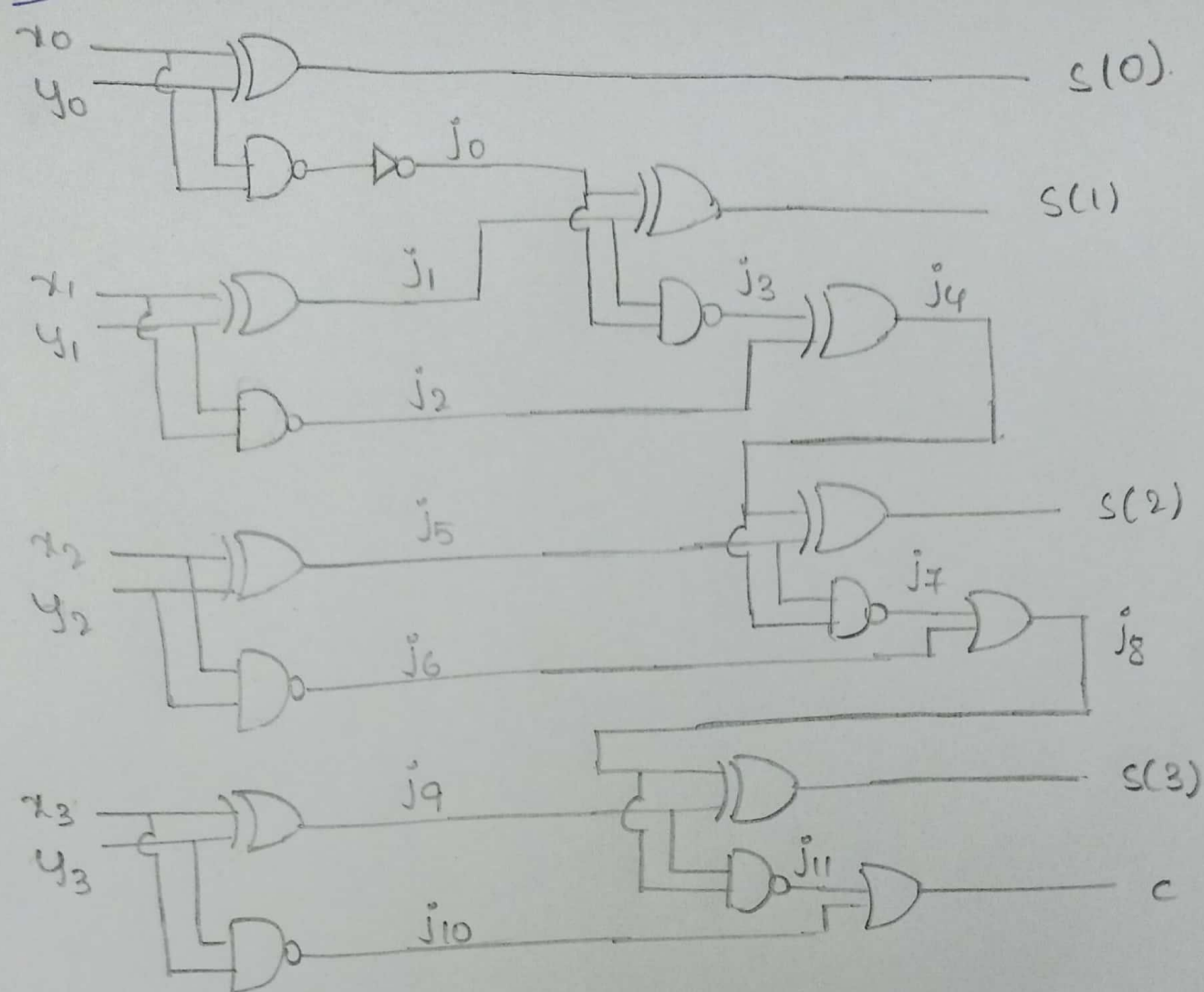

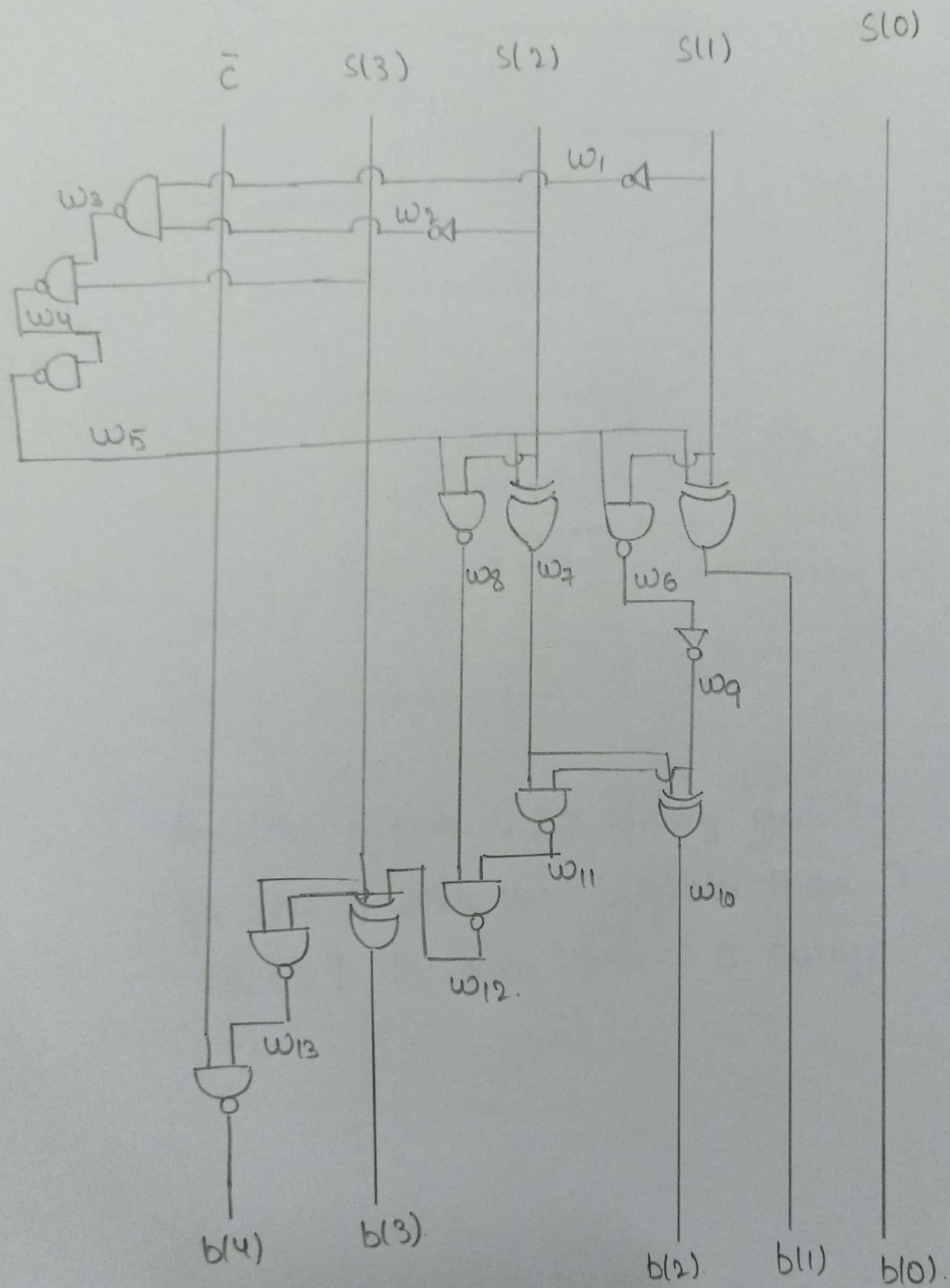Here we perform 4 bit binary addition.
 We add 6 when sum is greater than 9.
 s(3:0) is the sum. and c is carry.



\bar{c} can be obtained from previous circuit.

5).


x and y are two single digit decimal integers, such that $x \geq y \geq 0$.

x and y are five bit binary form.


For single digit decimal integers BCD and binary subtraction will be same.

We can use half-subtractor for least significant bit ($y(0)$ and $x(0)$)

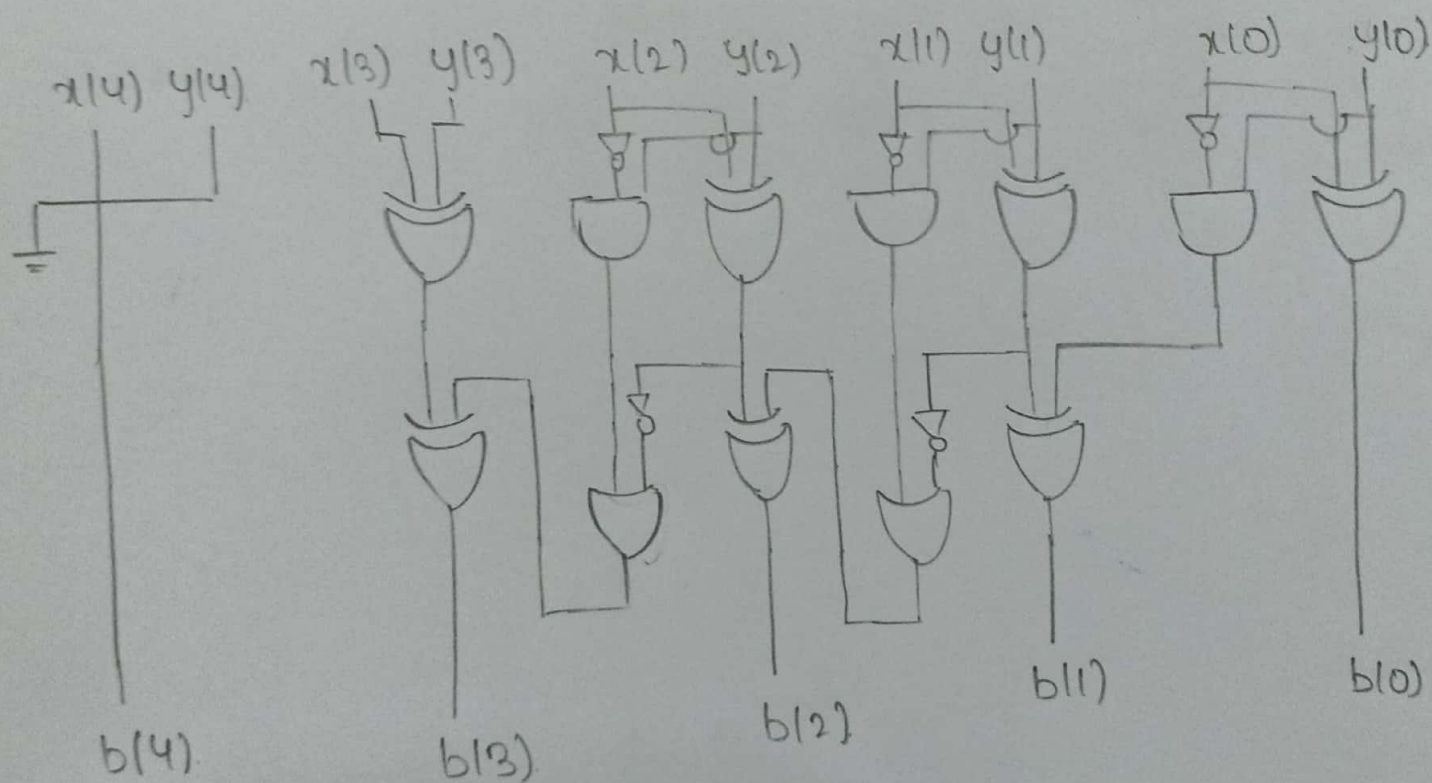Given $y \leq x$, there is no need of borrow circuit for MSB.



using required gates

 

For the 8,9 questions codes are presented below :

In the following, I have implemented the gate-level logic circuits using NOT, NAND, NOR, XOR and XNOR gates, and last four gates must be 2 i/p – 1 o/p gates. I re-used any of the results from the previous questions to a subsequent one just by representing the prior result by a Behavioral-level block diagram.

Problem 1) Suppose, you want to display a single-digit decimal non-negative integer (0 to 9) in a 7-segment LED display by selecting one of buttons numbered 0 to 9 in the input. Also suppose that, to perform addition and subtraction operations, you want to represent a single-digit decimal integer in binary coded decimal (BCD) form using four binary bits. So, you decided to first build a decimal to BCD encoder that will output the BCD in four-bit binary corresponding to one of the selected buttons. Assume that selecting a button corresponds to a logic 1. Build a gate-level logic circuit that will output a single-digit decimal integer in the BCD form depending on the selected number button.

Structural Verilog code :

```
module question1(Out,I9,I8,I7,I6,I5,I4,I3,I2,I1,I0);
input I9,I8,I7,I6,I5,I4,I3,I2,I1,I0;
output [3:0]Out;
wire [7:0]x;

//minimized code instead using multiple times primitive gates instantiation
nor g0(x[0],I1,I3),g1(x[1],I5,I7),g3(x[3],I9,x[2]),g5(x[4],I2,I3),g6(x[5],I6,I7),g8(x[6],I4,I5),g10(x[7],I9,I8);
nand g2(x[2],x[0],x[1]),g7(Out[1],x[4],x[5]),g9(Out[2],x[6],x[5]);
not g4(Out[0],x[3]),g11(Out[3],x[7]);
endmodule
```

Test bench

```
module question1_tb;
// Inputs
    reg I9,I8,I7,I6,I5,I4,I3,I2,I1,I0;
// Outputs
    wire [3:0] Out;
// Instantiate the Unit Under Test (UUT)
```

```

question1 uut (.Out(Out), .I9(I9), .I8(I8), .I7(I7), .I6(I6), .I5(I5), .I4(I4), .I3(I3), .I2(I2), .I1(I1),
.I0(I0));

initial begin

    // Initialize Inputs

    I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;

    #100 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 1;

    #100 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 1;I0 = 0;

    #100 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 1;I1 = 0;I0 = 0;

    #100 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 1;I2 = 0;I1 = 0;I0 = 0;

    #100 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 1;I3 = 0;I2 = 0;I1 = 0;I0 = 0;

    #100 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 1;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;

    #100 I9 = 0;I8 = 0;I7 = 0;I6 = 1;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;

    #100 I9 = 0;I8 = 0;I7 = 1;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;

    #100 I9 = 0;I8 = 1;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;

    #100 I9 = 1;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;

    #100 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;


    #100 $finish ;

end

end module

```

Timing diagram :

 

Behavioral Verilog code :

```
module question1_beh(Out,I9,I8,I7,I6,I5,I4,I3,I2,I1,I0);
input I9,I8,I7,I6,I5,I4,I3,I2,I1,I0;
output [3:0]Out;
reg [3:0]Out;
always@(*)
    case({I9,I8,I7,I6,I5,I4,I3,I2,I1,I0})
        // I-9876543210 bits order
        10'b1000000000 : Out = 4'b1001;
        10'b0100000000 : Out = 4'b1000;
        10'b0010000000 : Out = 4'b0111;
        10'b0001000000 : Out = 4'b0110;
        10'b0000100000 : Out = 4'b0101;
        10'b0000010000 : Out = 4'b0100;
        10'b0000001000 : Out = 4'b0011;
        10'b0000000100 : Out = 4'b0010;
        10'b0000000010 : Out = 4'b0001;
        10'b0000000001 : Out = 4'b0000;
    endcase
endmodule
```

Test bench

```
module question1_beh_tb;
// Inputs
    reg I9,I8,I7,I6,I5,I4,I3,I2,I1,I0;
// Outputs
    wire [3:0] Out;
// Instantiate the Unit Under Test (UUT)
    question1_beh uut (.Out(Out),
        .I9(I9),.I8(I8),.I7(I7),.I6(I6),.I5(I5),.I4(I4),.I3(I3),.I2(I2),.I1(I1),.I0(I0));
```

```

initial begin

    // Initialize Inputs

    I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;
#10 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 1;
#10 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 1;I0 = 0;
#10 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 1;I1 = 0;I0 = 0;
#10 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 1;I2 = 0;I1 = 0;I0 = 0;
#10 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 1;I3 = 0;I2 = 0;I1 = 0;I0 = 0;
#10 I9 = 0;I8 = 0;I7 = 0;I6 = 0;I5 = 1;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;
#10 I9 = 0;I8 = 0;I7 = 0;I6 = 1;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;
#10 I9 = 0;I8 = 0;I7 = 1;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;
#10 I9 = 0;I8 = 1;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;
#10 I9 = 1;I8 = 0;I7 = 0;I6 = 0;I5 = 0;I4 = 0;I3 = 0;I2 = 0;I1 = 0;I0 = 0;


#50 $finish;

end

endmodule

```

Timing diagram :

 

Problem 2) Now, for the LED display, assume that the logic output 1 is needed for any of these seven segments in the display to light up the corresponding LED. Build a gate-level logic circuit that will display a single-digit decimal integer in the BCD form to symbolic form in 7-segment LED display.

Structural Verilog code :

```
module question2(a,b,c,d,e,f,g,A);

input [3:0]A;

wire [3:0]Abar;

output a,b,c,d,e,f,g;

wire [18:0]x;

not n[3:0](Abar[3:0],A[3:0]);

not inv(x[3],x[8]);

xor g0(x[0],A[0],A[2]),g1(x[2],A[1],A[0]);

nor nr1(x[1],A[3],A[1]),nr2(x[4],Abar[1],A[0]),nr3(x[12],e,x[11]),nr4(x[9],Abar[2],A[1]),

nr5(x[15],x[9],x[13]),nr6(x[16],x[14],A[3]),nr7(x[14],A[1],A[0]),nr8(x[13],Abar[2],A[0]),nr9(x[17],x[3],

A[3]),nr10(x[18],x[13],x[9]);

nand

nd1(a,x[0],x[1]),nd2(b,x[2],A[2]),nd3(c,x[4],Abar[2]),nd4(x[6],Abar[2],Abar[0]),nd5(x[7],A[1],Abar[0]),

nd6(e,x[6],x[7]),nd7(d,x[12],Abar[3]),nd8(x[11],x[8],x[10]),nd9(x[8],A[1],Abar[2]),nd10(x[10],x[9],A[0]),

nd11(f,x[15],x[16]),nd12(g,x[17],x[18]);

endmodule
```

Test bench

```
module question2_tb;

// Inputs
reg [3:0] A;

// Outputs
wire a,b,c,d,e,f,g;

// Instantiate the Unit Under Test (UUT)
question2 uut (.a(a),.b(b),.c(c),.d(d),.e(e),.f(f),.g(g),.A(A));

initial begin
```



```


        // Initialize Inputs

        A = 4'd0;
#100 A = 4'd1;
#100 A = 4'd2;
#100 A = 4'd3;
#100 A = 4'd4;
#100 A = 4'd5;
#100 A = 4'd6;
#100 A = 4'd7;
#100 A = 4'd8;
#100 A = 4'd9;
#100 A = 4'd0;

    end
endmodule

```

Timing diagram :

 

Behavioral Verilog code :

In this code we considered abcdefg as [6:0]Y

```

module question2_beh(Y,A);

    input [3:0]A;

    output [6:0]Y;

    reg[6:0]Y;

```

```

always@(A)
begin
    case(A)
        4'b0000: Y = 7'b11111110;
        4'b0001: Y = 7'b01100000;
        4'b0011: Y = 7'b11111001;
        4'b0010: Y = 7'b1101101;
        4'b0110: Y = 7'b1011111;
        4'b0111: Y = 7'b11100000;
        4'b0101: Y = 7'b1011011;
        4'b0100: Y = 7'b0110011;
        4'b1000: Y = 7'b1111111;
        4'b1001: Y = 7'b1111011;
        4'b1101: Y = 7'b1011011;
        default Y=7'b00000000;
    endcase
end
endmodule

```

Test Bench :

```

module question2_beh_tb;
// Inputs
    reg [3:0] A;
// Outputs
    wire [6:0] Y;
// Instantiate the Unit Under Test (UUT)
    question2_beh uut (.Y(Y),.A(A));
initial begin
    // Initialize Inputs
    #100 A = 4'd0;
    #100 A = 4'd1;

```

```

#100 A = 4'd2;

#100 A = 4'd3;

#100 A = 4'd4;

#100 A = 4'd5;

#100 A = 4'd6;

#100 A = 4'd7;

#100 A = 4'd8;

#100 A = 4'd9;


#100 A = 4'd0;

    end

endmodule

```

Timing diagram:

 

Problem 3) Given two single-digit non-negative decimal integers x and y in the BCD form, build a gate-level logic circuit that will compare the two input integers. There will be 3 logic outputs, and one of these will be logic 1 and all others will be 0 depending on $x > y$, $x < y$, or $x = y$.

Structural Verilog code :

In this code we considered x, y as m, n

```

module question3(m,n,Y);

input [3:0]m,n;

output [2:0]Y;

wire [3:0]mbar,nbar;

wire [27:0]w;

not n0[3:0](mbar,m),n1[3:0](nbar,n);

xnor xn[3:0](w[3:0],m,n);

```

```

nand
nd1(w[5],w[2],w[3]),nd2(w[4],w[1],w[0]),nd3(w[7],m[2],nbar[2]),nd4(w[12],w[1],w[29]),nd5(w[13],
m[0],nbar[0]),nd6(w[9],w[2],w[3]),nd7(w[10],m[1],nbar[1]),nd8(Y[1],w[15],w[16]),nd9(w[19],mbar[2],
n[2]),nd10(w[21],mbar[1],n[1]),nd11(w[23],mbar[0],n[0]),nd12(Y[2],w[26],w[27]);

nor
nr1(Y[0],w[5],w[4]),nr2(w[6],n[3],mbar[3]),nr3(w[8],w[28],w[7]),nr4(w[14],w[12],w[13]),nr5(w[11],w
[9],w[10]),nr6(w[24],w[12],w[23]),nr7(w[15],w[6],w[8]),nr8(w[16],w[11],w[14]),nr9(w[17],x[3],nbar[
3]),nr10(w[18],w[30],w[19]),nr11(w[25],w[9],w[21]),nr12(w[27],w[17],w[18]),nr13(w[26],w[24],w[2
5]);

endmodule

```

Test bench:

```

module question3_tb;

// Inputs
    reg [3:0] m;
    reg [3:0] n;

// Outputs
    wire [2:0] Y;

// Instantiate the Unit Under Test (UUT)
    question3 uut (.m(m),.n(n),.Y(Y));

    initial begin

// Initialize Inputs
        m = 4'd3;n = 4'd0;

#100 m = 4'd6;n = 4'd6;

#100 m = 4'd6;n = 4'd9;

#100 m = 4'd3;n = 4'd6;


#100 m = 4'd9;n = 4'd9;

    end

endmodule

```

Timing diagram:

 

Behavioral Verilog code:

In this code we considered x,y as m,n

```
module question3_beh(m,n,Y);
```

```
input [3:0]m,n;
```

```
output [2:0]Y;
```

```
reg [2:0]Y;
```

```
always@(m,n)
```

```
begin
```

```
Y = 3'b0;
```

```
    if(m==n) Y[0] = 1;
```

```
    else if(m>n) Y[1] = 1;
```

```
    else Y[2] = 1;
```

```
end
```

```
endmodule
```

Test bench:

```
module question3_beh_tb;
```

```
// Inputs
```

```
    reg [3:0] m,n;
```

```
// Outputs
```

```
    wire [2:0] Y;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
    question3_beh uut (.m(m),.n(n),.Y(Y));
```

```
initial begin
```

```
// Initialize Inputs
```

```
    m = 4'd3;n = 4'd0;
```

```
#100 m = 4'd6;n = 4'd6;
```

```
#100 m = 4'd6;n = 4'd9;
```

```
#100 m = 4'd3;n = 4'd6;
```


```
#100 m = 4'd9;n = 4'd9;
```

```

end
endmodule

```

Timing diagram:

 

Problem 4) You want to perform addition operation on two single-digit decimal integers x and y (both can be positive or zero) in the BCD form. First, build a gate-level logic circuit which will be able to perform addition on x and y (you can use bit-wise or two-bit wise or direct four-bit addition) and will produce the result in a five-bit form. Now, build a gate-level circuit that will convert the five-bit binary result to BCD form so that it can be displayed using two 7-segment LED displays.

Structural Verilog code:

```

module bcdadders(b,x,y);

output [4:0]b;

input [3:0]x;

input [3:0]y;

wire [3:0]s;

wire c;

wire [12:0]j;

wire [13:0]w;

not n1(j[0],j[12]);

xor
g1(b[0],x[0],y[0]),g2(s[1],j[0],j[1]),g3(j[1],x[1],y[1]),g4(j[5],x[2],y[2]),g5(s[2],j[4],j[5]),g6(j[9],x[3],y[3]),
g7(s[3],j[8],j[9]),l1(j[4],j[2],j[3]),l2(j[8],j[6],j[7]);

xnor l3(c,j[10],j[11]);

nand
k1(j[12],x[0],y[0]),k2(j[2],x[1],y[1]),k3(j[3],j[0],j[1]),k4(j[7],j[4],j[5]),k5(j[6],x[2],y[2]),k6(j[10],x[3],y[3]),
k7(j[11],j[8],j[9]);

not n1(w[1],s[1]),n2(w[2],s[2]),n3(w[9],w[6]);

```

```

xor x1(b[1],s[1],w[5]),x2(w[7],w[5],s[2]),x3(b[2],w[7],w[9]),x4(b[3],s[3],w[12]);
nand nd1(w[3],w[1],w[2]),nd2(w[4],s[3],w[3]),nd3(w[5],w[4],c),nd4(w[6],w[5],s[1]),
    nd5(w[8],w[5],s[2]),nd6(w[11],w[7],w[9]),nd7(w[12],w[8],w[11]),nd8(w[13],s[3],w[12]),
    nd9(b[4],w[13],c);
endmodule

```

Test Bench:

```

module question4_str_tb;

// Inputs
reg [3:0] x;
reg [3:0] y;

// Outputs
wire [4:0] b;

// Instantiate the Unit Under Test (UUT)
question4_str uut (.b(b),.x(x),.y(y));

initial begin

// Initialize Inputs
#100 x = 4'b0; y = 4'b0;

#100 x = 4'd3;

#100 y = 4'd9;

#100 x = 4'd9;

#100 y = 4'd3;

#100 x = 4'd6;


#100 $finish;

end

endmodule

```

Timing diagram:

 

Behavioral Verilog code:

```
module question4_beh(sum,x,y);
input [4:0]x,y;
output [4:0]sum;
reg [4:0]sum,bcd;
always@(x,y)
begin
    sum= x+ y ;
    if(sum>9)
        bcd = sum + 5'b00110;
    else
        bcd = sum;
    end
endmodule
```

Test Bench:

```
module question4_beh_tb;
// Inputs
reg [4:0] x;
reg [4:0] y;
// Outputs
wire [4:0] sum;
// Instantiate the Unit Under Test (UUT)
question4_beh uut (.sum(sum),.x(x),.y(y));
initial begin
// Initialize Inputs
    x = 5'd1;y = 5'd3;
#100 x = 5'd3;y = 5'd6;
#100 x = 5'd3;y = 5'd6;
#100 x = 5'd9;y = 5'd6;
```



```
#100 x = 5'd6;y = 5'd6;
```


```
#100 x = 5'd7;y = 5'd6;
```

```
#100 x = 5'd9;y = 5'd6;
```

```
end
```

```
endmodule
```

Timing diagram:

 

Problem 5) You also want to perform subtraction operation on two single-digit decimal integers x and y ($x \geq y \geq 0$) represented in the BCD form. First, build a gate-level logic circuit which will be able to subtract a smaller non-negative number y from x, both of which are in five-bit binary form, and will produce a result in a five-bit binary form. Build a logic circuit, using the one you built or otherwise, to perform $x-y$ with x, y and $(x-y)$ in BCD form. (You can use any subtraction scheme.)

Structural Verilog code:

```
module question5(b,x,y);  
    input [4:0]x;  
    input [4:0]y;  
    output [4:0]b;  
    wire [15:1]w;  
    not n1(w[1],y[0]),n2(w[4],x[1]),n3(w[7],x[2]),n4(w[10],w[3]),n5(w[13],w[6]);  
    xor x1(b[0],x[0],y[0]),x2(w[3],x[1],y[1]),x3(w[6],x[2],y[2]),x4(w[9],x[3],y[3]),  
        x5(b[1],w[2],w[3]),x6(b[2],w[12],w[6]),x7(b[3],w[15],w[9]),x8(b[4],x[4],y[4]);  
    nand nd1(w[5],w[4],y[1]),nd2(w[8],w[7],y[2]),nd3(w[11],w[2],w[10]),  
        nd4(w[12],w[5],w[11]),nd5(w[14],w[12],w[13]),nd6(w[15],w[8],w[14]);  
    nor nr1(w[2],w[1],x[0]);  
endmodule
```

Test Bench:

```
module question5_tb;  
    // Inputs
```

```

reg [4:0] x;

reg [4:0] y;

// Outputs

wire [4:0] b;

// Instantiate the Unit Under Test (UUT)

question5 uut (.b(b),.x(x),.y(y));

initial begin

#100 x = 5'd4;y = 5'd3;

#100 x = 5'd9;

#100 y = 5'd6;

#100 x = 5'd7;


#100 $finish;

end

endmodule

```

Timing diagram:

 

Behavioral Verilog code:

```

module question5_beh(f,x,y);

input [4:0]x;

input [4:0]y;

output reg [4:0]f;

always@(*)

begin

```

```

        f = x - y;
end
endmodule

```

Test Bench:

```

module question5_beh_tb;

// Inputs
    reg [4:0] x;
    reg [4:0] y;

// Outputs
    wire [4:0] f;

// Instantiate the Unit Under Test (UUT)
    question5_beh uut (.f(f),.x(x),.y(y));

    initial begin

// Initialize Inputs
        #100 x = 5'd4;y = 5'd3;

        #100 x = 5'd9;

        #100 y = 5'd6;

        #100 x = 5'd7;

        #100 $finish;

    end

endmodule

```

Timing diagram:

